



This engineering note depicts how to wire up a tool touch plate to the MB-02V6 Breakout board. The inputs have been configured to be active when the input is at 0V by setting the *In Pullups* to 5V

Option 1

Preferred as the tool bit is connected to 0V via the alligator clip